

# Electrical Impedance Measurements: Algorithms for impedance estimation and equivalent circuit parameters determination



Pedro M. Ramos  
pedro.m.ramos@tecnico.ulisboa.pt

1


## Introduction

- What is electrical impedance?
- Why does it matter?
- How do we measure electrical impedance?
- How do we know the circuit of the measured impedance?

2
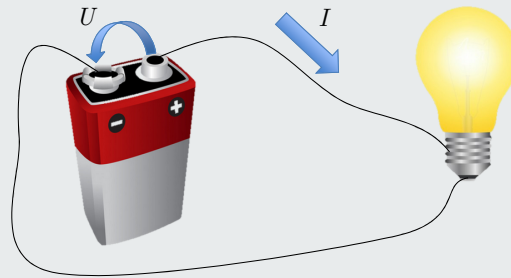
## What is electrical impedance?

- In DC (direct current), the relation between the voltage and the current applied to a conductor, is the electrical resistance.



$$I = \frac{U}{R}$$


$$R = \frac{U}{I}$$

- This is Ohm's law.


3
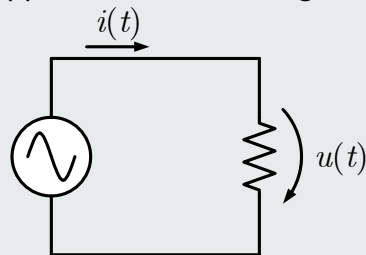
## What is electrical impedance?

- What happens when the voltage is a sinewave AC (from alternate current)?



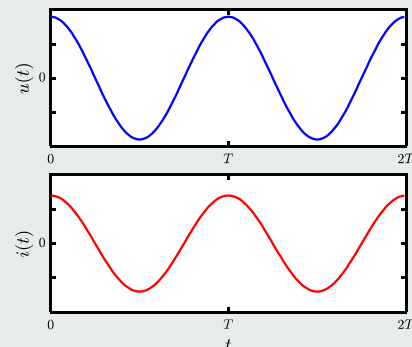
$$R = \frac{U_{RMS}}{I_{RMS}} \quad U_{RMS} = \sqrt{\frac{1}{T} \int_T u^2(t) dt}$$




4
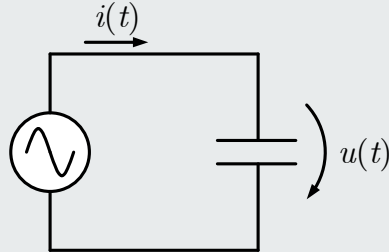
## What is electrical impedance?

- What if the resistor is replaced with a capacitor?



$$\frac{u(t)}{i(t)} = ?$$

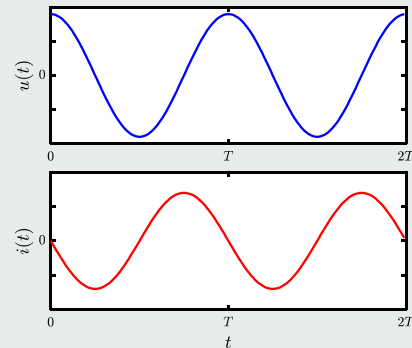

5

## What is electrical impedance?

- With sinewaves, it is better not to use  $u(t)$  and  $i(t)$  and use instead phasors.
- These are complex numbers that fully describe the sinewave

$$u(t) = U \cos(2\pi ft + \varphi_U) \quad \longrightarrow \quad \bar{U} = U e^{j\varphi_U}$$




$$i(t) = I \cos(2\pi ft + \varphi_I) \quad \longrightarrow \quad \bar{I} = I e^{j\varphi_I}$$

- The frequency  $f$  is implicit when phasors are used ( $\omega = 2\pi f$ ).
- $f$  is needed to go back from phasors to  $u(t)$  and  $i(t)$ .

6
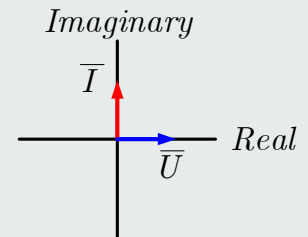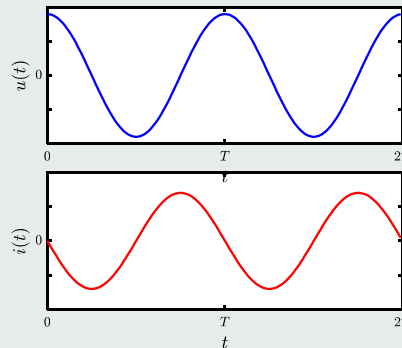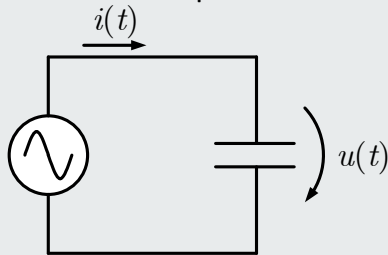
## What is electrical impedance?




- Back to the capacitor circuit. How/where are the phasors?



7

## What is electrical impedance?

- What if the load is now an inductor?

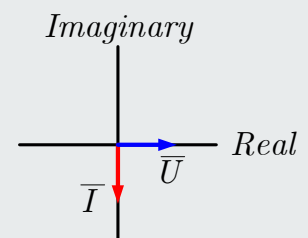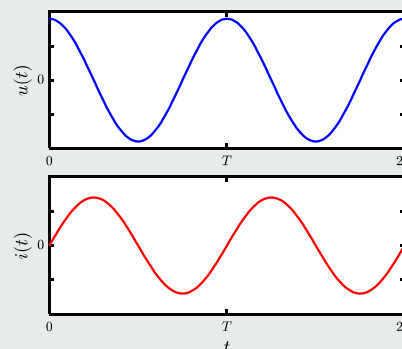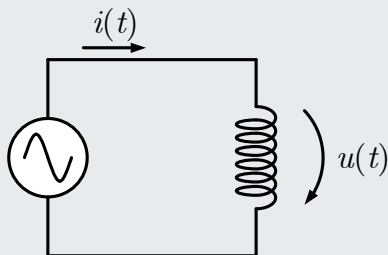

8

## What is electrical impedance?

- Electrical impedance can be defined with sinewave stimulus using the phasors







$$\bar{U} = U e^{j\varphi_U}$$

$$\bar{I} = I e^{j\varphi_I}$$

- The electrical impedance  $Z$  is

$$Z = \frac{\bar{U}}{\bar{I}} = \frac{U}{I} e^{j(\varphi_U - \varphi_I)} = |Z| e^{j\varphi_Z}$$


## What is electrical impedance?

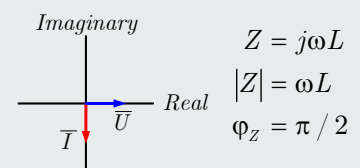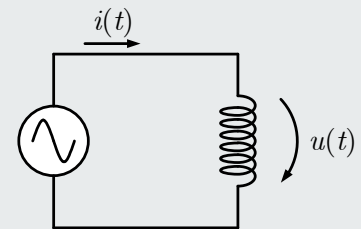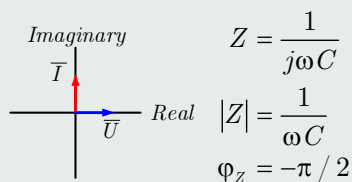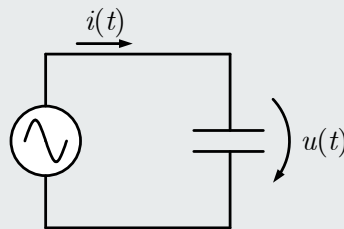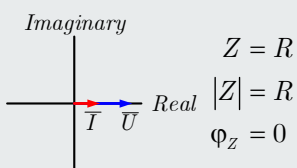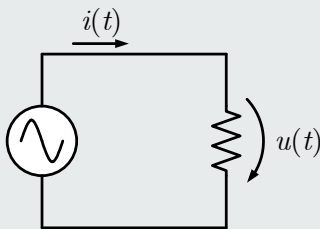

## What is electrical impedance?


- These basic elements can be combined. For example:

In series

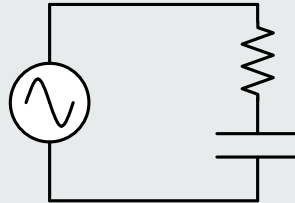

$$Z = Z_1 + Z_2 = R + \frac{1}{j\omega C}$$

In parallel

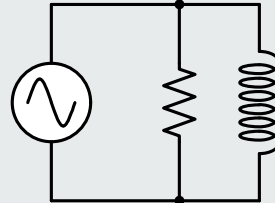

$$Z = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{j\omega RL}{R + j\omega L}$$

11

## Why does it matter?


- Some examples:
  - Electrical impedance is used in many sensors where the measurand changes the impedance frequency response of the sensor.
  - Bioimpedance is used in non-invasive test monitoring of living organisms.
  - In rechargeable battery systems, the battery output impedance can be used to estimate the battery SOH (state of health).

12


## Why does it matter?

- To derive, useful information from the impedance, it must be measured at different frequencies. Example, for a vibrating wire viscosity sensor:

Impedance frequency response

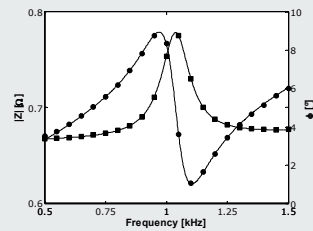

Nyquist Plot

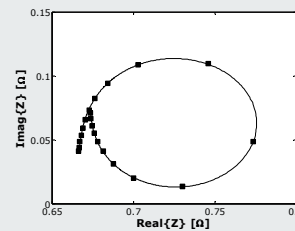


- Impedance Spectroscopy (IS)

13
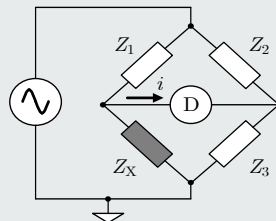
## How is electrical impedance measured?

- Pre-digital, impedance measurement methods included mostly bridges:




- Manual adjustment of  $Z_1$ ,  $Z_2$  and  $Z_3$  to cancel  $i$ , leads to  $Z_x = Z_1 Z_3 / Z_2$ .
- High level of expertise and experience required.
- Measuring many, many frequencies is almost impossible.

14


## How is electrical impedance measured?

- Evolution of analog electronics, ADCs and digital signal processors, have led to the development of highly efficient impedance measurement devices.

Auto-balancing bridge method

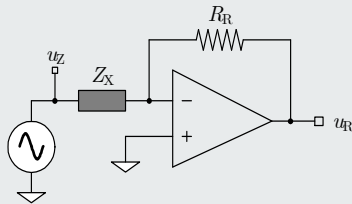

Voltage-current method

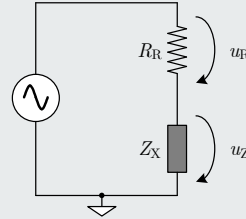

15

## How is electrical impedance measured?



- In these two measurement setups, ADCs acquire samples from two sinewave voltages.
- Algorithms estimate the sinewave parameters and from there, the impedance parameters ( $|Z|$  and  $\varphi_Z$ ) are estimated.
- The efficiency of these algorithms is crucial. This includes their uncertainty and also how long does the calculation require.

16


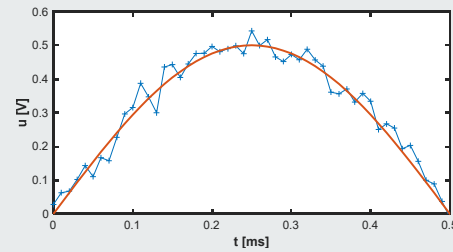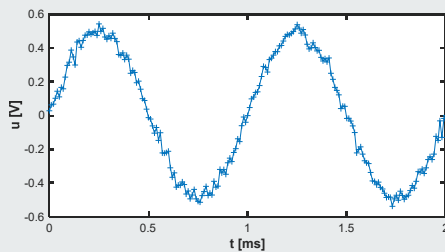
## How is electrical impedance measured?



- One algorithm that we have extensively used is sine-fitting.
- It estimates the sinewave parameters (amplitude, phase, DC component and frequency) of a set of acquired samples from a sinewave voltage.



17

## How is electrical impedance measured?

- Measurement setup


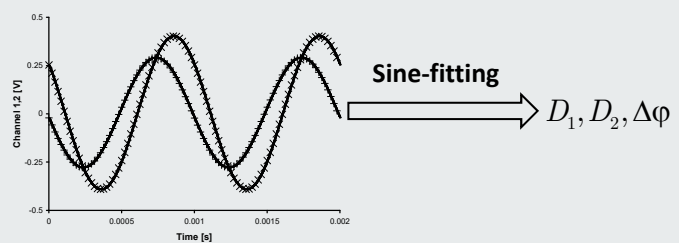
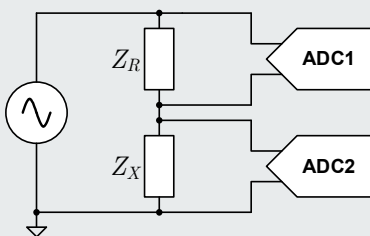


$$|Z_X| = \frac{D_2}{D_1} |Z_R| \quad \varphi_Z = \Delta\varphi + \varphi_{Z_R}$$

18
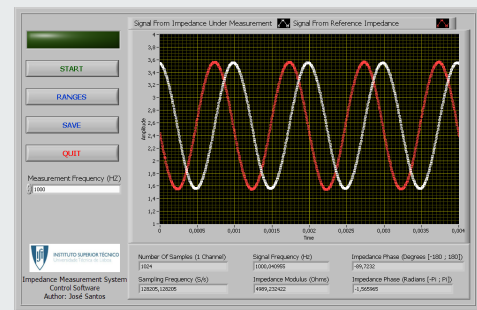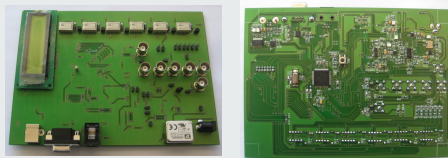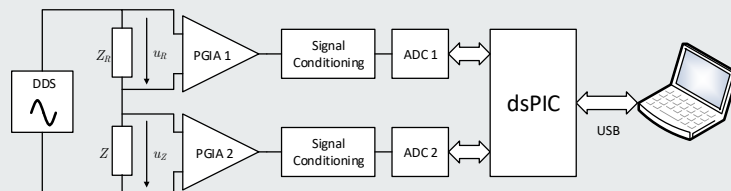
## How is electrical impedance measured?

- Implemented in a dsPIC based embedded measurement system.



19

## How is electrical impedance measured?

- How to measure the impedance frequency response?
- Method A: Single-tone sweep method**
  - Set the measurement frequency on the generator;
  - Acquire samples from both ADCs;
  - Use sine-fitting to estimate sinewave voltage parameters and from them, the impedance parameters (for that measurement frequency);
  - Repeat steps 1-3 for the next measurement frequencies.

20



## How is electrical impedance measured?

- How to measure the impedance frequency response?
- **Method B: Multi-harmonic method**
  1. Design multi-harmonic stimulus;
  2. Upload stimulus to arbitrary waveform generator (AWG);
  3. Acquire samples from both ADCs;
  4. Use multi-harmonic waveform fitting algorithm to estimate harmonic amplitude and phases of the acquired voltages and from them, the impedance parameters (at the frequencies of all harmonics).

21

## How is electrical impedance measured?

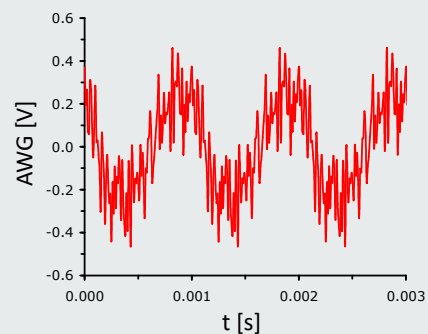
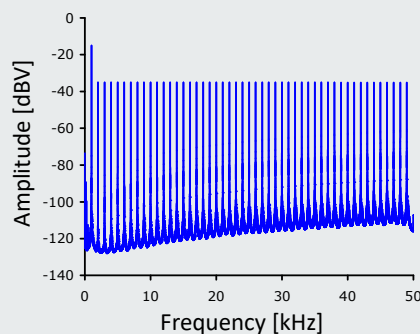
- Example 1:  $f = 1$  kHz, with higher fundamental and 48 lower amplitude harmonics



22
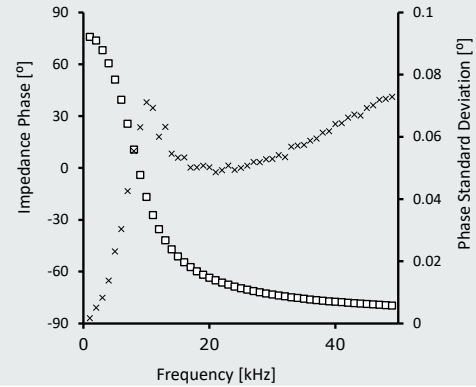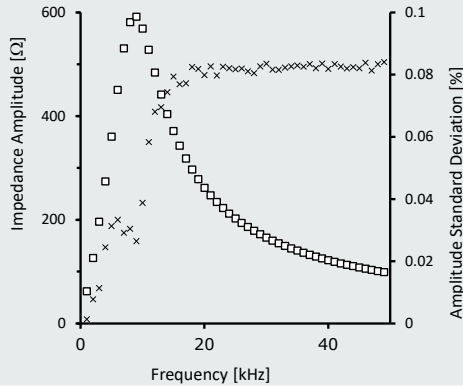
## How is electrical impedance measured?




- Results from example 1 with RLC parallel circuit with resonance near 9 kHz.



23

## How is electrical impedance measured?

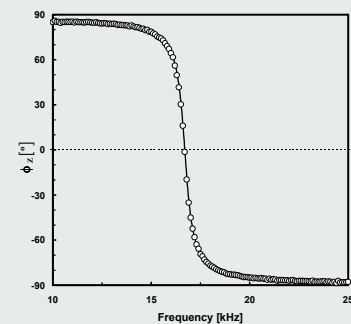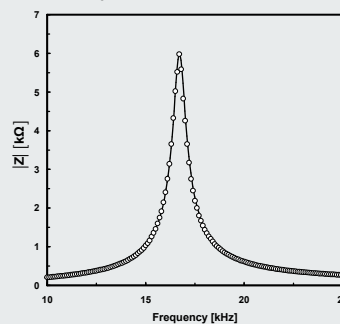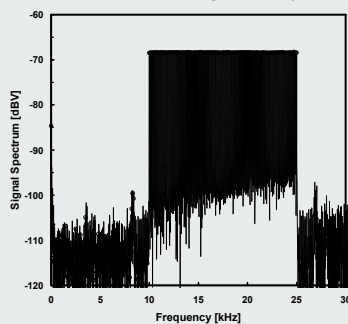- Example 2:  $f = 100$  Hz, without fundamental and 250 harmonics in the 10 kHz to 25 kHz range. Impedance is an LC parallel circuit.



24

## How do we know the impedance circuit?

- This is split into two parts:
  - Part 1: If the circuit topology is known, how do we estimate the circuit parameters?
  - Part 2: If the circuit topology is unknown, how do we determine the circuit topology?

25

## How to estimate the circuit parameters?

- Option 1: CNLS (Complex Nonlinear Least-Squares)
  - Developed by J. R. Macdonald.
  - It is a algorithm that, given a circuit topology, estimates the values of the components that best fit with the measured IFR.
  - It is a closed program with multiple circuit topologies.
  - Highly configurable but requires good initial estimates to converge to the correct circuit parameters.

26

## How to estimate the circuit parameters?

- Option 2: Genetic Algorithms (GAs)
  - Genetic algorithms can efficiently search a vast, multidimensional search space and find the approximate location of the absolute minimum.
  - To effectively search the multi-decade search space (associated with component values), the estimated value is the log 10 base value of the component value.
  - Requires many iterations and fine-tuning.

27

## How to identify the impedance circuit?

- Option 1: Vector Fitting (VF)
  - Estimates the coefficients of two polynomials whose ratio fits the measured Impedance Frequency Response (IFR).
  - It does not estimate directly the circuit topology.
- Option 2: Gene Expression Programming (GEP)
  - Evolutionary algorithm specifically used to obtain the circuit topology that best fits the measured IFR.


28

## How to identify the impedance circuit?


- Gene Expression Programming (GEP)

The circuit topology is described in a tree structure.

Example:

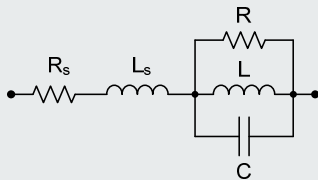

Operators	
R → 1	Series → +
L → 2	Parallel → //
C → 3	

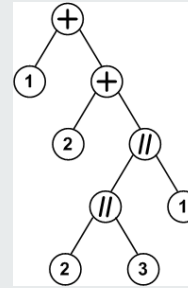

Gene	+	1	+	2	//	//	1	2	3
		R		L			R	L	C

29

## How to identify the impedance circuit?

- Gene Expression Programming (GEP)
  - A set of circuits (population) is evaluated to assess its fitness.
  - Each circuit is described by a Gene which is a sequence of elements.
  - There is a maximum sequence size.
  - To ensure that the sequence corresponds to a valid circuit, it has a head and a tail. The head has operators and components while the tail only has components.
  - GEP operations combine and change these sequences.

30


## How to identify the impedance circuit?

- Gene Expression Programming (GEP) Operations
  - Replication: a new population of circuits is obtained from the previous one based on their fitness.
  - Mutation: some random positions on a few random genes are changed.
  - Transposition: parts of the gene are copied to another location within the gene.
  - Recombination: pairs of randomly chosen genes exchange part of their gene code.
  - In mutation and transposition, care must be taken to ensure that GEP coding rules are maintained.
  - The best gene is always carried to next generation (survival of the fittest).

31

## How to identify the impedance circuit?

- Gene Expression Programming (GEP)

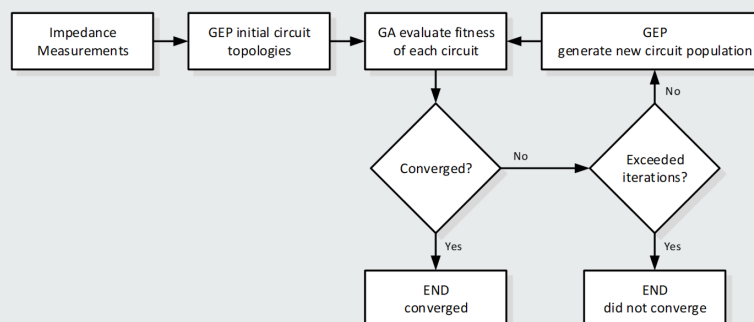


32


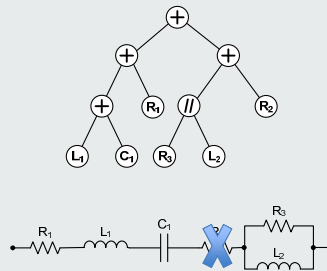
## How to identify the impedance circuit?

- Gene Expression Programming (GEP)
  - Simplification routine identifies components that can be removed from the circuit:




33

## How to identify the impedance circuit?

- Gene Expression Programming (GEP)
  - Using more complex circuit elements:



Series Combinations		Parallel Combinations	
Code	Type	Code	Type
12	R+L	-12	R//L
13	R+C	-13	R//C
23	L+C	-23	L//C
123	R+L+C	-123	R//L//C

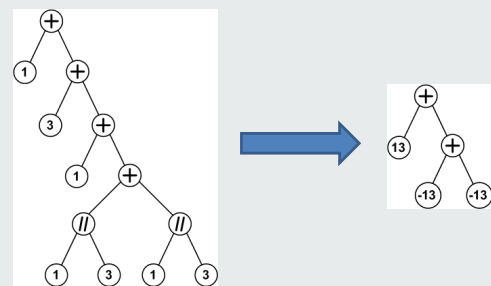

34
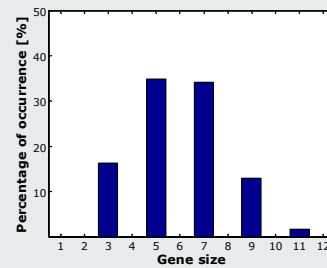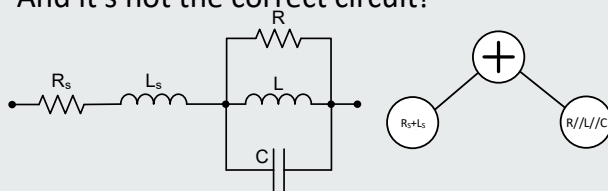
## How to identify the impedance circuit?


- Gene Expression Programming (GEP)
  - In most cases, with convergence, additional components are added to the gene.
  - These do not affect the impedance response at the measured frequency.
  - However, they appear as longer genes.
  - And it's not the correct circuit!



35
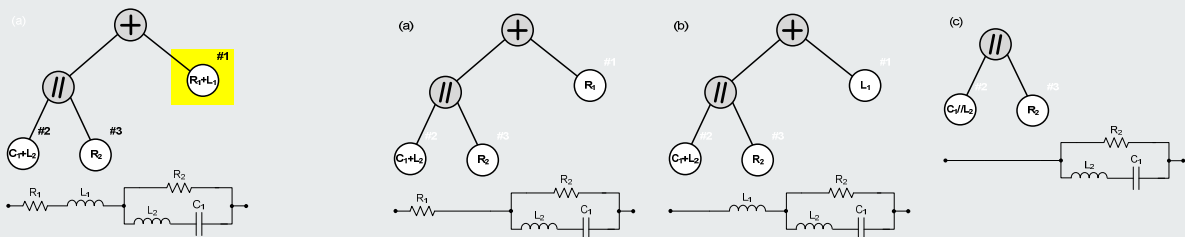
## How to identify the impedance circuit?


- Gene Expression Programming (GEP)
  - How to remove components that are not needed?



36
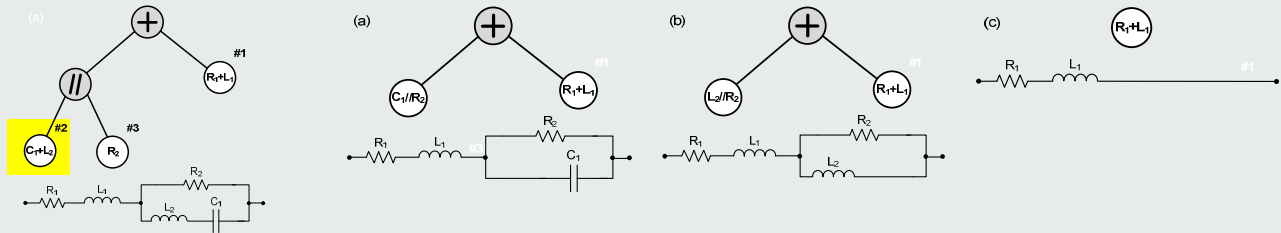
## How to identify the impedance circuit?


- Gene Expression Programming (GEP)
  - How to remove components that are not needed?



37
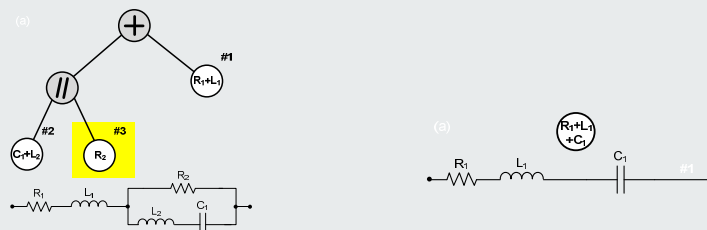
## How to identify the impedance circuit?



- Gene Expression Programming (GEP)
  - How to remove components that are not needed?



38
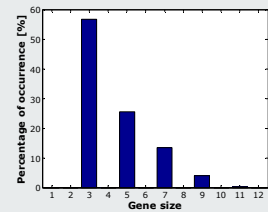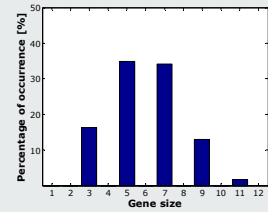
## How to identify the impedance circuit?




- Gene Expression Programming (GEP)
  - Has this process helped?
    - Average gene size 5.7 → 4.3.
    - Average number of iterations 6.9 → 3.8.
    - Convergence to correct circuit 15.6 % → 56.8 %.
    - Convergence 96 % → 100 %.



39
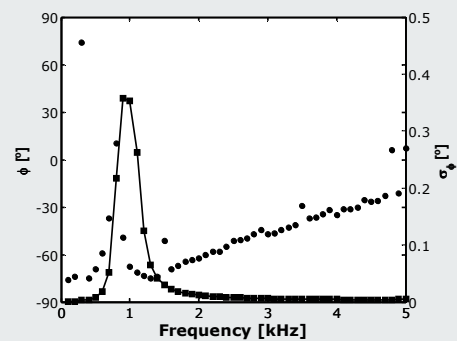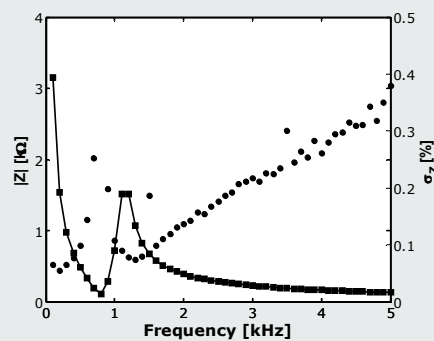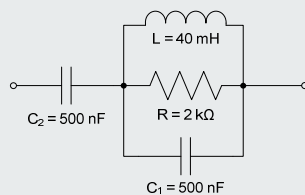
## How to identify the impedance circuit?




- Gene Expression Programming (GEP) MEASUREMENT results



40
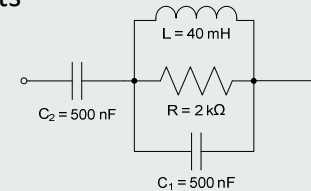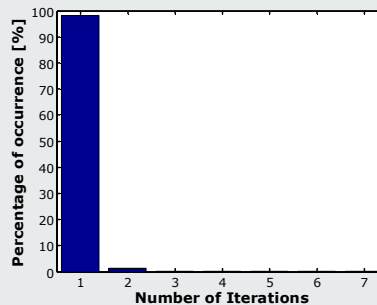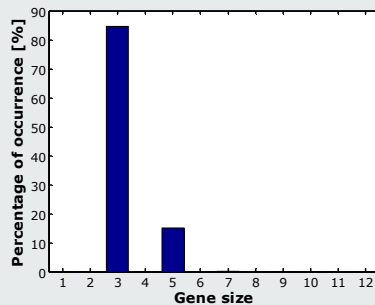
## How to identify the impedance circuit?

- Gene Expression Programming (GEP) MEASUREMENT results



Experimental standard deviation:

R: 0.11 %

C<sub>1</sub>: 0.06 %

L: 0.06 %

C<sub>2</sub>: 0.05 %

41


## How to identify the impedance circuit?

- Vector Fitting (VF)
  - The VF algorithm estimates the coefficients of two polynomials whose ratio fits the measured IFR.
  - The algorithm does not estimate the circuit topology.
  - However, from the polynomials an iterative procedure to retrieve the circuit topology has been developed.
  - This is still a work in progress....

42
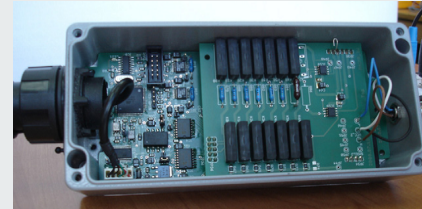
## Examples of embedded impedance measurement systems

- A Low Cost Miniaturized Impedance Analyzer (2010)
  - Based on two AD5933, 1 MHz, 12-bit impedance converter, network analyzer from Analog Devices.
  - Impedance range: 10  $\Omega$  up to 10 G $\Omega$ .
  - Frequencies: 0.01 Hz up to 100 kHz.
  - Maximum errors of 2 % and 2.5 °.




J. Hoja and G. Lentka, "Interface circuit for impedance sensors using two specialized single-chip microsystems", *Sensors and Actuators A: Physical*, vol. 163, pp. 191-197, 2010. doi: 10.1016/j.sna.2010.08.002

43
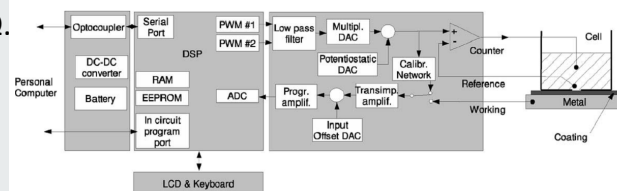
## Examples of embedded impedance measurement systems

- Seven-Decade Handheld-Impedance-Measurement System (2015)
  - Specifically designed for electrochemical measurements.
  - Processor MSP430 with 12-bit, 200 ks/s.
  - Impedance range: 100  $\Omega$  up to 100 G $\Omega$ .
  - Frequencies: 0.01 Hz up to 100 kHz.
  - Uncertainty of 5 % and 3 °.




E. Angelini, A. Carullo, S. Corbellini, F. Ferraris, V. Gallone, S. Grassini, M. Parvis and A. Vallan, "Handheld-impedance-measurement system with seven-decade capability and potentiostatic function", *IEEE Transactions on Instrumentation and Measurement*, vol. 55, no. 2, pp. 436-441, Apr. 2006. doi: 10.1109/TIM.2006.870103

44
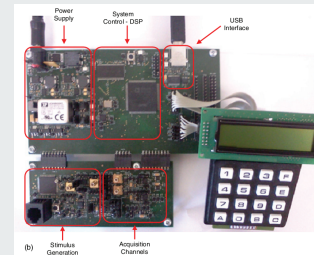
## Examples of embedded impedance measurement systems

- Embedded System for Viscosity Measurements (2015)
  - Based on a Analog Devices DSP with two external 16-bit ADCs with 1 MS/s.
  - Stimulus from a 14-bit DAC.
  - Frequencies: 100 Hz up to 10 kHz.
  - Multi-harmonic stimulus with multi-harmonic fit.
  - 4-wire connection to impedance.
  - Sensor has very low impedance (near 1  $\Omega$ ).



J. Santos, F. Janeiro and P. M. Ramos.  
"Development, implementation, and characterization of a standalone embedded viscosity measurement system based on the impedance spectroscopy of a vibrating wire sensor",  
Measurement Science and Technology, vol. 26, n.º 10, pp. 105903-1-14, Oct. 2015.  
doi: 10.1088/0957-0233/26/10/105903

45

## Conclusions

- Very old topic!
- Major recent developments within the field due to evolution of analog electronics, ADCs and portable low cost digital signal processing.
- Application in many fields.

46

## The end

- Thank you for your attention



Pedro M. Ramos

pedro.m.ramos@tecnico.ulisboa.pt

Google Scholar list of publications

